



## True RMS Converter Utilising TRAC

Ian Shaw

The TRAC family of totally reconfigurable Field Programmable Analog Devices offers an integrated path from signal processing problems to working silicon solutions - in minutes!

Introducing a Top-Down, Structured design discipline, TRAC enables rapid implementation, prototyping and product release. Rather than designing at the component level, TRAC champions a Computational Approach. Using eight simple mathematical building-blocks, any transfer function can be implemented on TRAC, and more besides!

With a combination of programmable silicon and design software, TRAC brings a truly Integrated Route to signal processing problem solving, providing designers with benefits formerly associated only with programmable digital devices, and offering a path to Custom Silicon for higher volume users.


### Introduction

True RMS conversion is normally performed by an expensive dedicated chip. This application note demonstrates the adaptability of TRAC in performing this function adapting a computational approach.

The RMS value of a waveform is the

Root of the **M**ean of the **S**quared value and is sometimes needed to calculate the power dissipated in a component. For example if a pulsed waveform has peak of 10 Amps and a duty cycle of 10:1 then clearly the average current would be 1 Amp. The RMS current, on the other hand, would be the true RMS value

$$\sqrt{\frac{10^2}{10}} = 3.16 \text{ Amps}$$

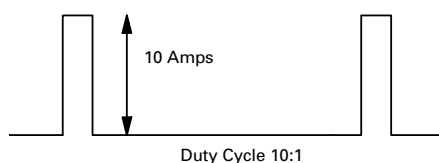


**Figure 1**  
**Typical Peak Rectifier Transformer Current Waveform**

This could be the typical current waveform in a mains transformer when followed by a rectifier and smoothing capacitor. The diode only conducts on the voltage peaks and large capacitor values result in narrow conduction angles.

In this example the average current of 1 Amp would result in power dissipation in the transformer winding ( $I^2R$ ) ten times higher than might be expected at first sight.

## Theory of Application

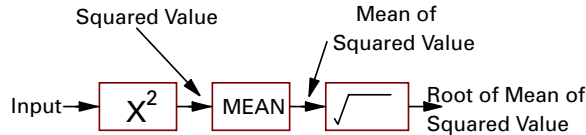


**Figure 2**  
**RMS Conversion Block Diagram**

The RMS value is achieved by squaring the input signal, taking the mean value and finally the square root. This is shown diagrammatically in Figure 2.

The basic TRAC implementation of the RMS converter is shown in Figure 3. First the waveform is transformed into the log domain and then doubled. This effectively squares the input since doubling in the log domain is the equivalent of squaring in the linear domain.

An antilog function transforms the waveform back into the linear domain and the mean value is derived using a single pole filter.

Finally the waveform is transferred to the log domain and halved which is the equivalent of taking the square root in the linear domain. The final antilog function transforms the waveform to the linear domain resulting in the square root of the mean of the squared input.

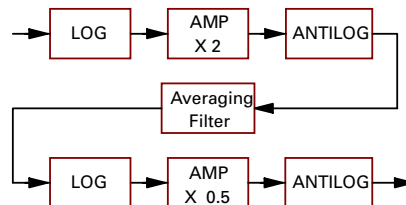

**Figure 3**  
**Block Diagram of TRAC Configuration**

## Software

The TRAC implementation is shown in Figure 4 and uses two TRAC ICs. Additions to the block diagram given in Figure 3 include a scaling voltage which is added/subtracted at the inputs to the log/antilog functions as appropriate to keep the cells within their operating range. This is achieved by adding a fixed DC voltage of one volt to I/O pin 26. A nominal one volt is also applied to I/O 36 but in the practical version this is adjusted to give the correct RMS DC output voltage. It performs both the function of scaling voltage and practical tolerance adjustment.

All TRAC functions, with the exception of the NIP (Non Inverting Pass) and the OFF function, invert the waveform applied with respect to the input which explains various NEG functions used to re-invert waveforms in the design.

TRAC Application Note AN7  
Issue 1 September 1998


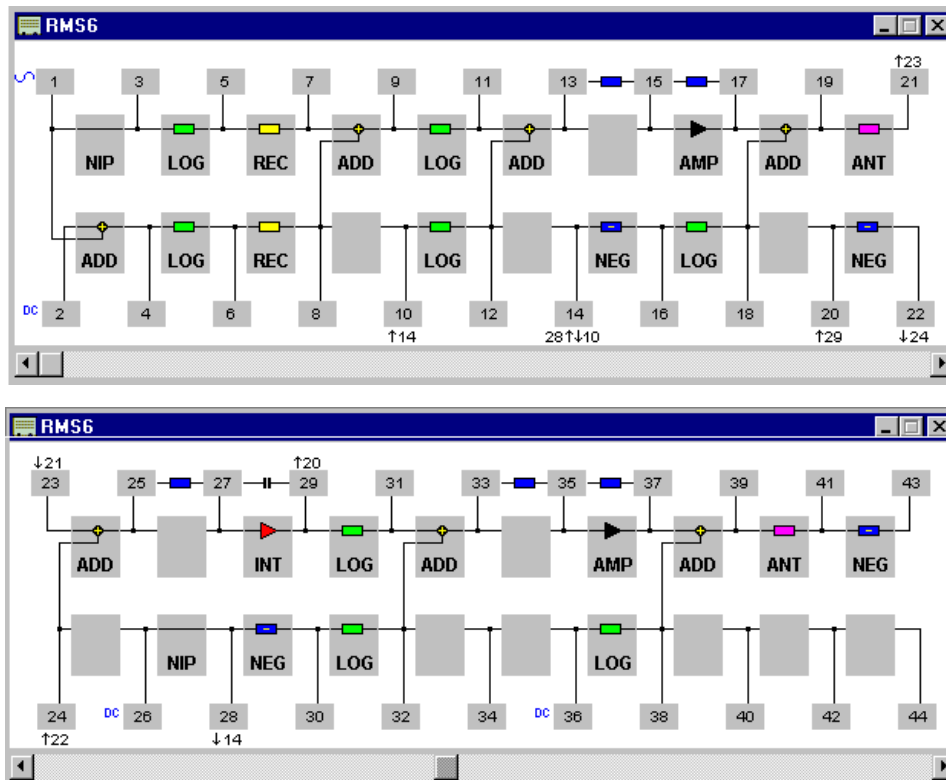


Figure 4  
TRAC True RMS to DC Design

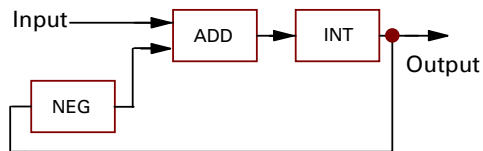

**Figure 5**  
**TRAC Software Implementation of Low Pass Filter**

The input section comprises a full wave rectifier function which includes a suitable dc input I/O 2 used to adjust the two halves of the rectified input waveform for equal amplitude. This is needed to ensure that practical tolerances in the LOG-REC function do not result in errors in the final RMS value. Inputs not greater than  $\pm 100$  mV should be used.

A filter function is required to achieve the mean value of the waveform and this is shown in Figure 5.


Figure 6 shows the input waveform and the output from I/O 43. The output can be seen to ramp up to the correct DC RMS value of the input waveform and a slight ripple will be observed. The latter can be removed by judicious choice of resistor

and capacitor in the filter. This in turn will increase the time taken to reach the final value which would usually be of no consequence in a practical circuit since this takes place in the first few hundred cycles required to average the waveform.

### Hardware

In addition to applying an input waveform and the trim and scaling voltages, it is necessary to define the gain of the two amplifier functions and the integrator using external components.

Suitable values for the first amplifier (gain = 2) are  $R_{input} = 1.5k\Omega$  and  $R_{feedback} = 3.0k\Omega$

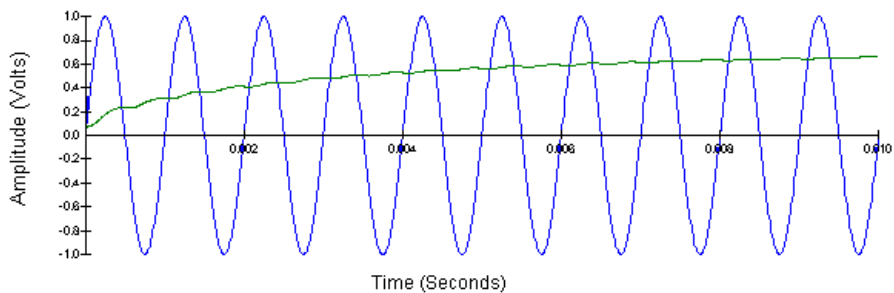

**Figure 6:**  
**Input and Output Waveforms**

**TRAC Application Note AN7**  
**Issue 1 September 1998**

---

Suitable values for the second amplifier (gain = 0.5) are  $R_{input} = 3.0k\Omega$  and  $R_{feedback} = 1.5k\Omega$

Suitable values for the filter are  $R = 3.0k\Omega$  and  $C = 680nF$

These are only suggested values in this application. In practice values in the range 1k - 100 k $\Omega$  would be suitable.

The filter values are dependant on the frequency of the input waveform and the values given are suitable for frequencies above 1 kHz. For lower

frequencies it will be necessary to increase the capacitor value to reduce the ripple content of the output DC RMS level.

To set up the converter in practice, it is recommended that a sine wave of 1 volt peak is applied to I/O 1 and the full wave rectified waveform, viewed on I/O 9, adjusted for equal heights on alternate peaks.

Finally the nominally 1 volt DC on I/O 36 is adjusted to give the correct DC RMS of 707 mV on I/O 43.

NOTES:

NOTES:

**TRAC Application Note AN7  
Issue 1 September 1998**

---

**NOTES:**

Fast Analog Solutions Ltd.  
Fields New Road, Chadderton, Oldham, OL9 8NP, United Kingdom.  
Tel: (+44) (0) 161 622 4567 Fax: (+44) (0) 161 622 4568  
e-mail: [trac@fas.co.uk](mailto:trac@fas.co.uk) Internet: <http://www.fas.co.uk>

**ZETEX**

**FAS**

TRAC products are supported by agents and distributors in many countries of the world. Details can be found on our web site.

A ZETEX GROUP COMPANY

This publication is issued to provide outline information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned. The Company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.

---

**TRAC**

TAN7-8